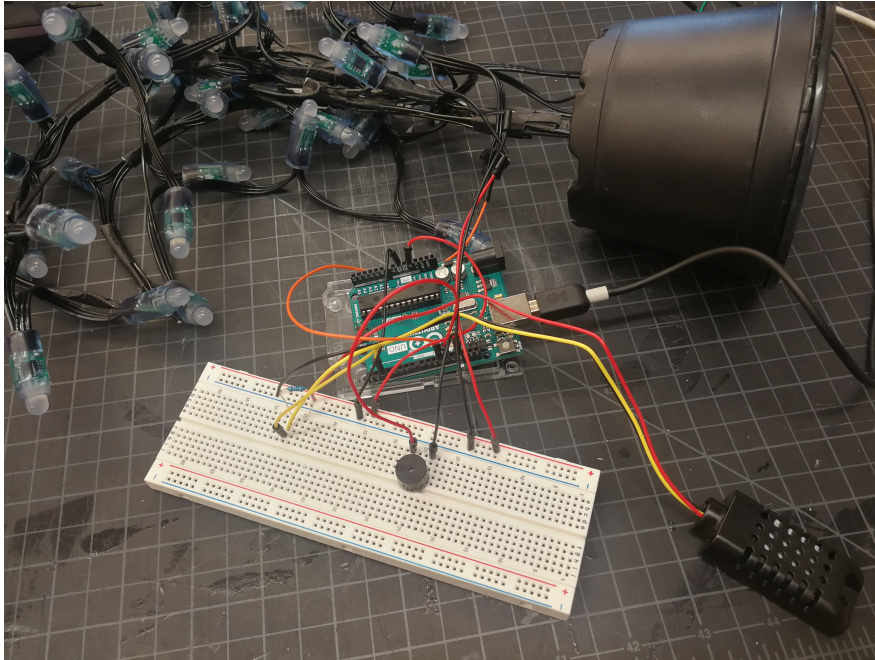


### 1. Add Buzzer to the Circuit



## 2. Schematics for Midterm Project

